

Built-In Self-Test Architectures

Proposed problems

Oprițoiu Flavius
flavius.oprițoiu@cs.upt.ro

November 22, 2024

Problem 1


Design a D type flip-flop having asynchronous, active low, set and reset inputs. The asynchronous set input has higher priority compared to the reset input. The interface of the flip-flop is the following:

```
1 module d_ff (
2     input clk,      //clock input
3     input rst_b,   //reset input, clears flip-flop
4     input set_b,   //set input, sets flip-flop
5     input d,        //synchronous data line
6     output reg q  //flip-flop output
7 );
```


Note: no testbench is required

 Problem 2

Construct the architecture for module *lfsr5b* depicted below:




Determine the periodicity of output sequence using a testbench generating the inputs like in the timing diagram below:

 

 Problem 3

Construct the architecture for module *sisr4b* depicted bellow:



Note: no testbench is required

Problem 4


Build a module called *check* having one input *i* on 5 bits and one output *o* on 1 bit. The output is active if the unsigned number at the input is a multiple of 8. The module's interface is presented below:

```
1 module check (
2     input [4:0] i ,
3     output o
4 );
```

Note: no testbench is required

 Problem 5

Construct the architecture for module *bist* depicted bellow:



Test the unit with a testbench generating the inputs like in the timing diagram bellow:

