

# Hardware design of a Sign-Magnitude sequential multiplier

Oprițoiu Flavius  
flavius.oprițoiu@cs.upt.ro

December 9, 2023

# Introduction


## Objectives:

- ▶ Construct a sequential architecture for Sign-Magnitude multiplication

## Architecture's characteristics:

- Operate fractional numbers on 8 bits
- Design and customize multiplier's components
- Design the control path of the architecture
 
# Sign-Magnitude sequential multiplier architecture



**Note:** Except `rst_b`, all other signals are *synchronous*.

# Register M (solved)

Stores the multiplicand, having the following interface:

- ▶ ld\_ibus: loads multiplicand's value from INBUS
  - ▶ ibus: the INBUS lines
- ▶ q: register's content

```
1 module reg_m(  
2     input clk , rst_b , ld_ibus , [7:0] ibus ,  
3     output reg [7:0] q  
4 );  
5     always @ (posedge clk , negedge rst_b)  
6         if (!rst_b)                      q <= 0;  
7         else if (ld_ibus)                q <= ibus;  
8     endmodule
```

# Register Q

Stores the multiplier, having the following interface:

- ▶ clr\_lsb: clear register's LSB
- ▶ ld\_ibus: loads multiplier's value from INBUS
  - ▶ ibus: the INBUS lines
- ▶ sh\_r: right shifts the register's content
  - ▶ sh\_i: bit to be loaded into MSB during right shift
- ▶ ld\_ibus: deliver accumulator's content onto OUTBUS
  - ▶ obus: the OUTBUS lines
- ▶ q: register's content

```
1 module reg_q(
2     input clk , rst_b , clr_lsb , ld_ibus , ld_ibus , sh_r ,
3     input sh_i , [7:0] ibus ,
4     output reg [7:0] obus , [7:0] q
5 );
6     always @ (posedge clk , negedge rst_b )
7         //treat inputs rst_b , clr_lsb , ld_ibus , sh_r here
8
9     always @ (*) //write content to obus when ld_ibus==1
10        obus = (ld_ibus) ? q : 8'bz;
11 endmodule
```

# Register A

Multiplier's accumulator, it has the following interface:

- ▶ clr: synchronous, active high reset
- ▶ ld\_sum: loads adder's result into accumulator
  - ▶ sum: adder's result to be loaded into accumulator
- ▶ ld\_sgn: loads accumulator's sign
  - ▶ sgn: accumulator's sign
- ▶ ld\_obuf: unload accumulator's content onto OUTBUS
  - ▶ obus: the OUTBUS lines
- ▶ sh\_r: right shift register's content
  - ▶ sh\_i: bit to be loaded into MSB during right shift
- ▶ q: accumulator's content

```
1 module reg_a(  
2     input clk , rst_b , clr , sh_r , ld_sgn , ld_obuf , ld_sum ,  
3     input sh_i , sgn , [7:0] sum ,  
4     output reg [7:0] obus , [7:0] q  
5 );  
6     //implementation here  
  
8     //write content to obus  
9 endmodule
```


# Control Unit

The control unit has the following interface:

- ▶ bgn: starts the multiplication
- ▶ q\_0: register Q's LSB
- ▶ cnt\_is\_7: active if COUNTER's value is 7
- ▶ c0: clears registers A and COUNTER, loads M from INBUS
- ▶ c1: loads Q from INBUS
- ▶ c2: loads adder's result back into A
- ▶ c3: right-shifts A concatenated with Q (introduce a bit of 0 in register A's MSB), increments COUNTER
- ▶ c4: sets sign of register A, clear register Q's LSB
- ▶ c5/c6: deliver register A/Q to OUTBUS
- ▶ fin: marks multiplication completion, activated along c5, c6

```
1 module ctrl_u(
2     input clk, rst_b, bgn, q_0, cnt_is_7,
3     output c0, c1, c2, c3, c4, c5, c6, fin
4 );
5     //implementation here
6 endmodule
```

## Control Unit (contd.)

 

**Important:** Control unit must be triggered by the opposite edge of the clock, compared to all the other sequential elements in the architecture!

# Putting together all the components

The Sign-Magnitude sequential multiplier's architecture:

```
1 module sm_unit (
2     input clk, rst_b, bgn, [7:0] ibus,
3     output fin, [7:0] obus
4 );
5     //implementation here
6 endmodule
7
8 module sm_unit_tb;
9     reg clk, rst_b, bgn; reg [7:0] ibus; wire fin; wire [7:0] obus;
10
11    sm_unit test (.clk(clk), .rst_b(rst_b), .bgn(bgn), .ibus(ibus),
12                  .fin(fin), .obus(obus));
13    localparam CLK_PERIOD=100, CLK_CYCLES=17, RST_PULSE=25;
14    localparam X=8'b10010111/*=-23*2^(-7)*/, Y=8'b10000011; /*=-3*2^(-7)*/
15    initial begin clk=1'd0; repeat (CLK_CYCLES*2) #(CLK_PERIOD/2) clk=~clk; end
16    initial begin rst_b=1'd0; #(RST_PULSE); rst_b=1'd1; end
17    initial begin bgn=1'd1; #200; bgn=1'd0; end
18    initial begin ibus=0; #100 ibus=X; #100 ibus=Y; end
19 endmodule
```

Testbench keeps OUTBUS in high impedance until 1300 time units, when, for 1 clock cycle OUTBUS becomes 8'b00000000, than, for another clock cycle, OUTBUS becomes 8'b10001010 only to remain in high impedance afterwards.