

# Hardware design of a Sign-Magnitude sequential multiplier

Proposed problems

Oprîtoiu Flavius  
flavius.opritoiu@cs.upt.ro

December 9, 2023

# Problem 1

Implement register Q of the Sign-Magnitude sequential multiplier architecture.

Start from the template below (available [here](#)):

```
1  module reg_q(  
2      input clk, rst_b, clr_lsb, ld_ibus, ld_obus, sh_r,  
3      input sh_i, [7:0] ibus,  
4      output reg [7:0] obus, [7:0] q  
5  );  
6      always @ (posedge clk, negedge rst_b)  
7          //treat inputs rst_b, clr_lsb, ld_ibus, sh_r here  
  
9      always @ (*) //write content to obus when ld_obus==1  
10         obus = (ld_obus) ? q : 8'bz;  
11 endmodule
```

## Problem 2

Construct register A of the Sign-Magnitude sequential multiplier architecture.

Start from the template below (available [here](#)) knowing that content's writing to the Outbus is constructed in a similar manner to register Q's.

```
1  module reg_a(  
2      input  clk, rst_b, clr, sh_r, ld_sgn, ld_obus, ld_sum,  
3      input  sh_i, sgn, [7:0] sum,  
4      output reg [7:0] obus, [7:0] q  
5  );  
6      //implementation here  
  
8      //write content to obus  
9  endmodule
```

## Problem 3

Build Sign-Magnitude sequential multiplier architecture's control unit, starting from the template below (available [here](#)).

```
1 module ctrl_u(  
2     input  clk, rst_b, bgn, q_0, cnt_is_7,  
3     output c0, c1, c2, c3, c4, c5, c6, fin  
4 );  
5     //implementation here  
6 endmodule
```

## Problem 4

Complete the Sign-Magnitude sequential multiplier architecture starting from the template below (available [here](#)), which includes a testbench for multiplying operands  $-23 * 2^{-7}$  and  $-3 * 2^{-7}$ .

```
1 module sm_unit (
2     input clk, rst_b, bgn, [7:0] ibus,
3     output fin, [7:0] obus
4 );
5     //implementation here
6 endmodule

8 module sm_unit_tb;
9     reg clk, rst_b, bgn; reg [7:0] ibus; wire fin; wire [7:0] obus;

11     sm_unit test (.clk(clk), .rst_b(rst_b), .bgn(bgn), .ibus(ibus),
12                 .fin(fin), .obus(obus));
13     localparam CLK_PERIOD=100, CLK_CYCLES=17, RST_PULSE=25;
14     localparam X=8'b10010111/*=-23*2-7*/, Y=8'b10000011;/*=-3*2-7*/
15     initial begin clk=1'd0; repeat (CLK_CYCLES*2) #(CLK_PERIOD/2) clk=~clk; end
16     initial begin rst_b=1'd0; #(RST_PULSE); rst_b=1'd1; end
17     initial begin bgn=1'd1; #200; bgn=1'd0; end
18     initial begin ibus=0; #100 ibus=X; #100 ibus=Y; end
19 endmodule
```