## Karnaugh Maps: Problems

For problems 1, 2 and 3, for each function (if possible !), implement with gates in VHDL the initial function and the minimized function, and compare them by simulation.

- 1. Using Karnaugh maps, find a minimal sum-of-products expression for each of the following logic functions. Indicate the distinguished 1-cells in each map.
  - (a)  $F = \sum_{X,Y,Z} (1,3,5,6,7)$
  - (b)  $F = \sum_{W,X,Y,Z} (1, 4, 5, 6, 7, 9, 14, 15)$
  - (c)  $F = \prod_{W,X,Y} (1,4,5,6,7)$
  - (d)  $F = \sum_{W,X,Y,Z} (0, 1, 6, 7, 8, 9, 14, 15)$
  - (e)  $F = \prod_{A,B,C,D} (4, 5, 6, 13, 15)$
  - (f)  $F = \sum_{A,B,C,D} (4, 5, 6, 11, 13, 14, 15)$
- 2. Using Karnaugh maps, find a minimal sum-of-products expression for each of the following logic functions. Indicate the distinguished 1-cells in each map. Find the complete sum for the logic functions from (d) and (e).
  - (a)  $F = \sum_{A,B,C} (0, 1, 2, 4)$
  - (b)  $F = \sum_{W,X,Y,Z} (1, 4, 5, 6, 11, 12, 13, 14)$
  - (c)  $F = \prod_{A,B,C} (1,2,6,7)$
  - (d)  $F = \sum_{W,X,Y,Z} (0, 1, 2, 3, 7, 8, 10, 11, 15)$
  - (e)  $F = \sum_{W,X,Y,Z} (1, 2, 4, 7, 8, 11, 13, 14)$
  - (f)  $F = \prod_{A,B,C,D} (1,3,4,5,6,7,9,12,13,14)$
- 3. Re-do the prime-number-detector minimization, assuming that 1 is not a prime number.

Problems with don't care input combinations.

- 4. Using Karnaugh maps, find a minimal sum-of-products expression for each of the following logic functions. Indicate the distinguished 1-cells in each map. Find all prime implicants and the essential prime implicants.
  - (a)  $G = \sum_{W,X,Y,Z} (0, 1, 3, 5, 14) + d(8, 15)$
  - (b)  $G = \sum_{W,X,Y,Z} (0, 1, 2, 8, 11) + d(3, 9, 15)$
  - (c)  $G = \sum_{A,B,C,D} (4, 6, 7, 9, 13) + d(12)$
  - (d)  $G = \sum_{A,B,C,D} (1, 5, 12, 13, 14, 15) + d(7, 9)$
  - (e)  $G = \sum_{W,X,Y,Z} (4,5,9,13,15) + d(0,1,7,11,12)$
- Re-do the minimization for the prime-number-detector for BCD (binary codded decimally) numbers, considering that 1 is not a prime number. Problems with product of sums:
- 6. Using Karnaugh maps, find a minimal product of sums expression for each of the logic functions from exercises 1 and 2.