


Optional

Logic families: CMOS family

Doru Todinca

Department of Computers
Politehnica University of Timisoara

CMOS logic levels and noise intervals

 


Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Figure 1 : CMOS logic levels and noise margins

- ▶ Figure 1 shows the logic levels for CMOS circuits in function of V_{CC} . Usually $V_{CC} = 5.0V$, but it can be smaller.
- ▶ LOW and HIGH mean 0 and 1

- ▶ V_{OLmax} is the maximum output voltage that an output in 0 logic can have
- ▶ V_{ILmax} is the maximum voltage at an input that is still considered to be a 0 logic
- ▶ $V_{ILmax} - V_{OLmax}$ is the noise margin for 0 logic.
- ▶ For 1 logic, the output voltage is at least V_{OHmin} , but an input is recognized as 1 if it is $\geq V_{IHmin}$
- ▶ Noise margin for 1 logic:
 $V_{OHmin} - V_{IHmin}$

Model of the MOS transistor

 


Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Figure 2 : Model of the MOS transistor as a voltage-controlled resistance

There are two type of MOS transistors: NMOS (with n channel) and PMOS (with p channel).

- ▶ A MOS transistor is a three terminal device
- ▶ An input voltage V_{IN} applied to one terminal controls the resistance between the other two terminals
- ▶ In digital circuits the resistance of the MOS transistor is
 - ▶ either very high, and the transistor is “OFF”
 - ▶ or very low, and the transistor is “ON”

The n MOS transistor

 

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Figure 3 : The N MOS transistor

- ▶ The terminals of a MOS transistor are called *gate*, *source* and *drain*
- ▶ The drain of an NMOS transistor is normally at a higher voltage than the drain
- ▶ The voltage from gate to source, V_{gs} is normally zero or positive.
- ▶ If $V_{gs} = 0$ then the resistance from drain to source, R_{ds} is very high (1 megohm or more). The transistor is “OFF”
- ▶ When V_{gs} increases, the resistance R_{ds} is very low (≤ 10 ohms) and the voltages in drain and source are almost equal (the transistor is “ON”)

The p MOS transistor


 


Figure 4 : The p MOS transistor

- ▶ The p-channel MOS transistor works similarly, but the source is normally at a higher voltage than the drain
- ▶ and normally $V_{gs} \leq 0$
- ▶ If $V_{gs} = 0$ the resistance R_{ds} is very high (10^6 ohms), i.e., the transistor is “OFF”
- ▶ If V_{gs} decreases algebraically (i.e. $V_{gs} < 0$), then R_{ds} decreases to a very low value and the transistor is “ON”: the voltage from drain and source are almost equal.

CMOS NOT gate

 

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

(b)

V_{IN}	$Q1$	$Q2$	V_{OUT}
0.0 (L)	off	on	5.0 (H)
5.0 (H)	on	off	0.0 (L)

(c)

 


Figure 5 : CMOS NOT gate (inverter): (a) circuit diagram; (b) functional behaviour; (c) logic symbol

CMOS NOT gate


1. If $V_{IN} = 0.0$ V:

- ▶ the NMOS transistor Q1 is OFF because $V_{gs} = 0$
- ▶ the PMOS transistor Q2 is ON because V_{gs} is a large negative value (-5.0 V)
- ▶ It means that Q2 presents only a small resistance between the power supply terminal V_{DD} and the output terminal V_{OUT}
- ▶ It results that $V_{OUT} = 5.0$ V

2. If $V_{IN} = 5.0$ V:

- ▶ Q2 is off because $V_{gs} = 0.0$ V.
- ▶ Q1 is on, since $V_{gs} = 5.0$ V (V_{gs} is large positive)
- ▶ Hence Q1 presents a small resistance between the output terminal and the ground
- ▶ Then, the output voltage is 0 V.

CMOS NOT gate

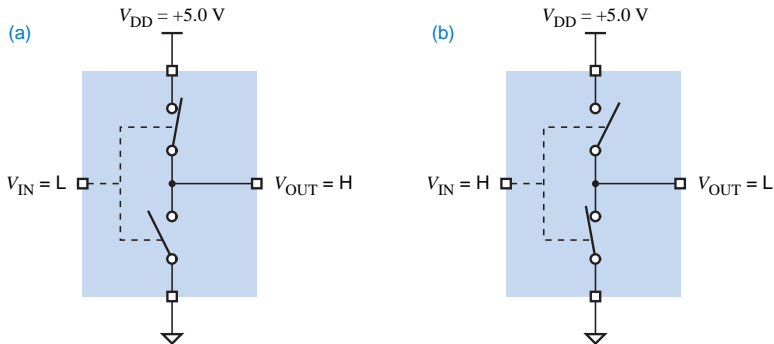


Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Figure 6 : Switch model for CMOS NOT gate: (a) LOW input; (b) HIGH input

CMOS NOT gate: switch model

- ▶ Figure 6 uses switches for modeling the behaviour of an CMOS inverter
- ▶ In the left part of the figure (a) the n-channel transistor (bottom) is modeled by a normally-open switch
- ▶ The p-channel transistor (top) is modeled by a normally-closed switch
- ▶ If we apply a HIGH voltage to V_{IN} the switches go to the opposite position (as shown in (b))
- ▶ Based on the switch model we use new symbols for the NMOS and PMOS transistors (in figure 7): PMOS has an inversion bubble at the gate terminal, suggesting that it is ON when V_{IN} is LOW (when V_{IN} is negative).


CMOS NOT gate

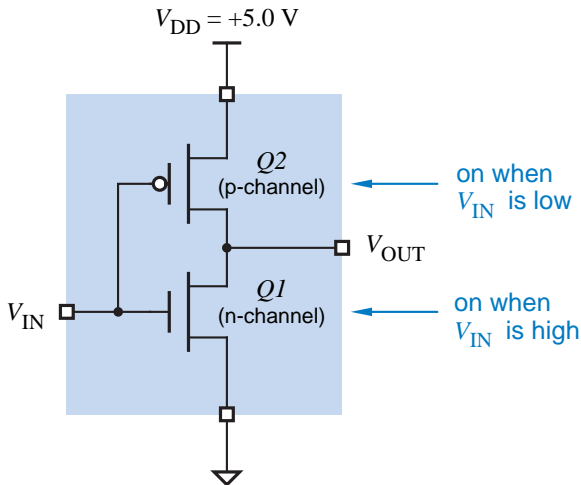

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Figure 7 : CMOS NOT gate, different CMOS transistors symbols

CMOS NAND

 

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

(b)

A	B	Q1	Q2	Q3	Q4	Z
L	L	off	on	off	on	H
L	H	off	on	on	off	H
H	L	on	off	off	on	H
H	H	on	off	on	off	L

(c)

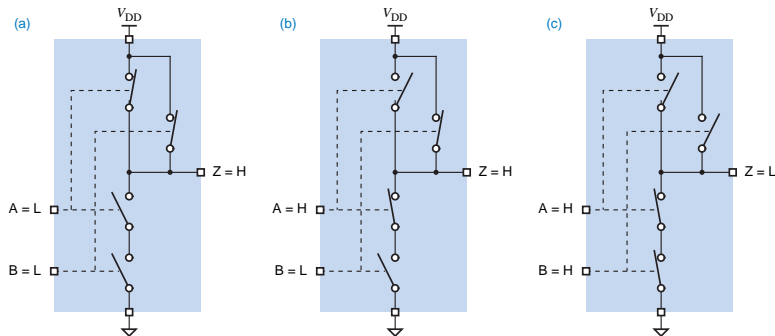


Figure 8 : CMOS 2-inputs NAND gate: (a) circuit diagram; (b) function table; (c) symbol

CMOS NAND

- ▶ Circuit diagram of CMOS NAND gate is shown in figure 8
- ▶ When at least one input is LOW (0.0 V):
 - ▶ the corresponding PMOS transistor(s) will be ON and a path is open between V_{DD} to output Z
 - ▶ It results that Z is HIGH
 - ▶ The path between Z and ground is blocked because at least one NMOS transistor is OFF
- ▶ When both inputs are HIGH (5.0 V):
 - ▶ both PMOS transistors are OFF
 - ▶ then, the path between V_{DD} and Z is blocked
 - ▶ but, both NMOS transistors are ON
 - ▶ which means that the path between ground and Z is open
 - ▶ hence Z is LOW
 - ▶ A switch model of the 2-inputs NAND gate is shown next (in fig 9)


CMOS NAND



Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Figure 9 : Switch model for CMOS 2-input NAND gate: (a) both inputs LOW; (b) one input HIGH and one LOW; (c) both inputs HIGH

CMOS NOR

 

(b)

A	B	$Q1$	$Q2$	$Q3$	$Q4$	Z
L	L	off	on	off	on	H
L	H	off	on	on	off	L
H	L	on	off	off	on	L
H	H	on	off	on	off	L

(c)



Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Figure 10 : CMOS 2-inputs NOR gate: (a) circuit diagram; (b) function table; (c) symbol


CMOS NOR

- ▶ Figure 10 (a) presents the circuit diagram of CMOS NOR gate
- ▶ There is a path between V_{DD} and Z only when both PMOS transistors are ON
- ▶ This happens only if all inputs are LOW
- ▶ If at least one input is HIGH then the corresponding NMOS transistor(s) is ON
- ▶ Which means that there is a path between ground and output Z, hence Z is LOW

CMOS gates

- ▶ The family is called CMOS (complementary MOS) because we use pairs of complementary transistors: one NMOS and one PMOS
- ▶ Of course, there can be gates with more than 2 inputs
- ▶ The CMOS gates have a naturally inverting behaviour
- ▶ In order to obtain non-inverting gates (i.e. AND and OR gates) an inverting level must be added to a NAND or NOR gate !
- ▶ It means that the non-inverting CMOS gates are slower (and more expensive) than inverting gates (NOT, NAND, NOR)

 Input-output transfer characteristic of a CMOS inverter



Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Figure 11 : Input-output transfer characteristic of a CMOS inverter